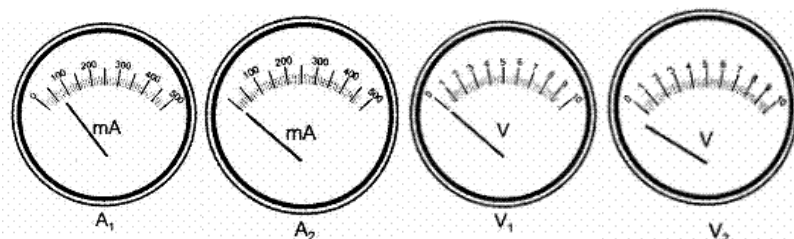


ELECTRICITY -06

Class 10 - Science


1. The positions of the pointer of the two ammeters A_1 and A_2 , and two voltmeters V_1 and V_2 available in the laboratory are shown in the given figure. For an experiment to study the dependence of the current on the potential difference across a resistor, the student would prefer

[1]




- a) ammeter A_2 and voltmeter V_1
 b) ammeter A_2 and voltmeter V_2
 c) ammeter A_1 and voltmeter V_1
 d) ammeter A_1 and voltmeter V_2
2. The correct set up for determining the equivalent resistance of two resistors R_1 and R_2 when connected in parallel is

[1]

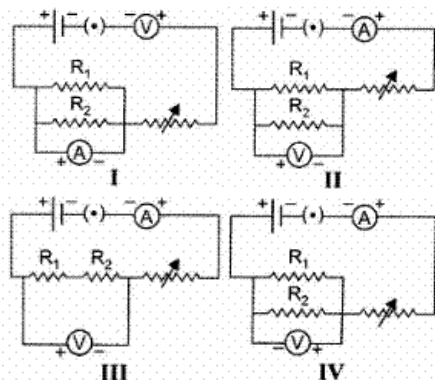


- a) I
 b) III
 c) IV
 d) II
3. Ramesh connects three resistors as shown below to find the equivalent resistance in series. The value measured by him should be close to

[1]

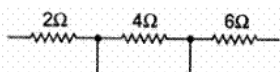

- a) $12\ \Omega$
 b) $8\ \Omega$
 c) $15\ \Omega$
 d) $10\ \Omega$
4. Two students A and B set up their circuits as shown below using identical values for the two resistors and all other devices.


[1]

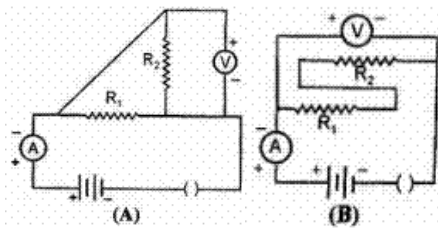

The observed readings of the ammeter and the voltmeter, by the two students are labelled as (i_A , V_A) and (i_B , V_B) respectively. The readings are likely to be related as


- a) ($i_A = i_B$); ($V_A < V_B$) b) ($i_A = i_B$); ($V_A > V_B$)
c) ($i_A = i_B$); ($V_A = V_B$) d) ($i_A > i_B$); ($V_A > V_B$)

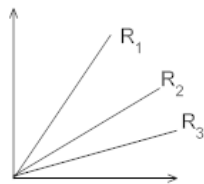5. A student carries out an experiment and plots the V-I graph of three samples of nichrome wire with resistances R_1 , R_2 and R_3 respectively figure. Which of the following is true? [1]




- a) $R_3 > R_2 > R_1$ b) $R_1 > R_2 > R_3$
c) $\left(R \propto \frac{1}{\text{slope of V-I graph}} \right)$ d) $R_3 = R_2 = R_1$

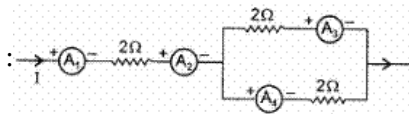6. The ammeters showing equal current in the following circuit are [1]




- a) A_3 and A_4 b) A_1 and A_2
c) A_2 , A_3 and A_4 d) A_1 , A_2 , A_3 and A_4

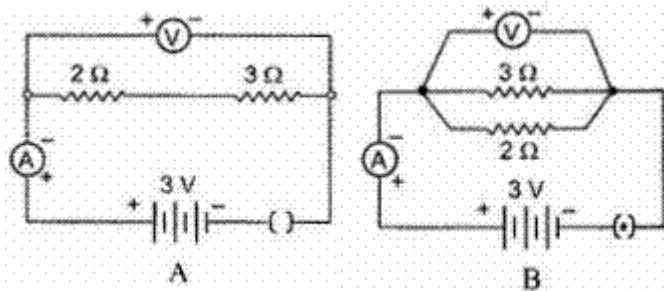7. For the circuits A and B shown below in a given figure, the voltmeter readings would be [1]



- a) 0.6 V in circuit A and 2.5 V in circuit B b) 0 V in both circuits
c) 5 V in both circuits d) 0 V in circuit A and 3V in circuit B.

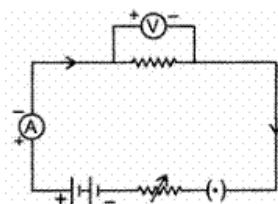8. The following circuit diagram shows the experimental set-up for the study of dependence of current on potential difference. which two circuit components are connected in series? [1]




a) Resistor and voltmeter

b) Ammeter and rheostat

c) Ammeter and voltmeter

d) Battery and voltmeter

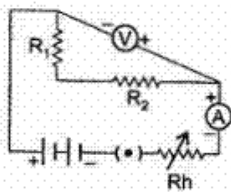9. For the experiment "to find the equivalent resistance of the two given resistors connected in parallel" the following circuit was drawn by a student. [1]



The teacher pointed out the possibility of the following faults :

- A. The ammeter was not correctly connected in the circuit.
- B. The voltmeter was not correctly connected in the circuit.
- C. The resistors R_1 and R_2 were not correctly connected in parallel.
- D. The rheostat and the key were not correctly connected in the circuit.

The two faults pointed out correctly by the teacher, are


a) B and C

b) D and A

c) A and B

d) C and D

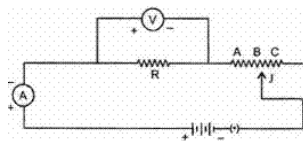10. To study the dependence of current (I) flowing on the applied potential difference (V) across a resistor, a student sets-up his apparatus as shown. He puts the sliding contact J , in the positions A, B and C, one by one and notes the three readings of the voltmeter as V_A, V_B, V_C and that of the ammeter as I_A, I_B, I_C . [1]



He would observe that


a) $V_A > V_B > V_C$ but $I_A > I_B > I_C$

b) $V_A = V_B = V_C$ but $I_A \neq I_B \neq I_C$

c) $V_A \neq V_B \neq V_C$ but $I_A = I_B = I_C$

d) $V_A = V_B = V_C$ but $I_A < I_B < I_C$

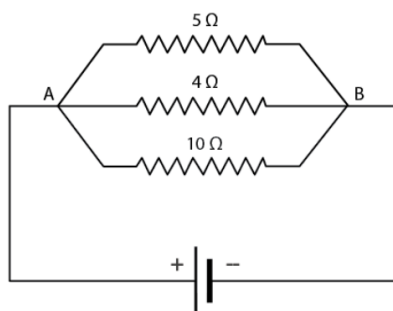11. In the circuit diagram given below, the current flowing across 5 ohm resistor is 1 amp. The current flowing through the other two resistors: [1]



a) 1.25 amp

b) None of these

c) 0.5 amp

d) 0.4 amp

12. Two resistances are connected in series as shown in the diagram. The potential difference across 12Ω resistor will be: [1]



-

-

-


a) $i_1 < i_2$; $V_1 < V_2$

b) $i_1 > i_2$; $V_1 > V_2$

c) $i_1 < i_2$; $V_1 = V_2$


d) $i_1 > i_2$; $V_1 = V_2$

- 4 / 20

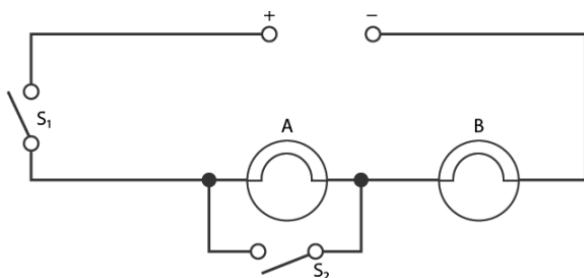


- a) When S_1 and S_2 are closed, lamps A and B are lit
- b) With S_2 open and S_1 closed A and B are lit
- c) With S_1 open and S_2 closed, A is lit and B is not lit
- d) With S_1 closed and S_2 open, lamp A remains lit even if lamp B gets fused

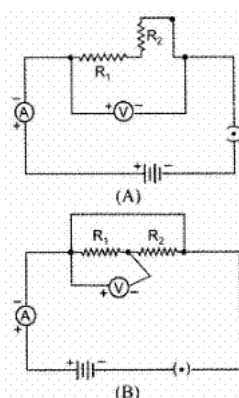17. Out of the two circuits shown here, the two resistors R_1 and R_2 have been correctly connected in series in [1]




- a) circuit A only
- b) circuit B only
- c) neither of the two circuits
- d) both circuits A and B

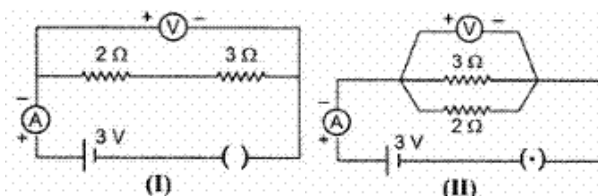18. For the two circuits I and II shown below, the voltmeter readings would be [1]



- a) 3 V in circuit I and 0 V in circuit II
- b) 0 V in circuit I and 3V in circuit II
- c) 3 V in both the circuits
- d) 0 V in circuit I and 2V in circuit II

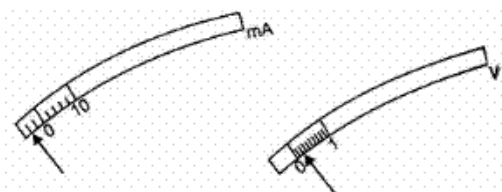
19. The rest positions of the needles in a Milliammeter and Voltmeter when not being used in a circuit are as shown in the figure. The 'zero error' and 'least count' of these two instruments are : [1]



- a) (-4 mA, +0.2 V) and (2 mA, 0.2 V) respectively
- b) (-4 mA, +0.2 V) and (1 mA, 0.1 V) respectively
- c) (+4 mA, -0.2 V) and (2 mA, 0.2 V) respectively
- d) (+4 mA, -0.2 V) and (1 mA, 0.1 V) respectively

20. To determine the equivalent resistance of a series combination of two resistors R_1 and R_2 , a student arranges the [1]


following set up :

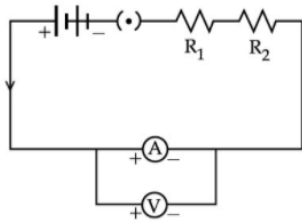


Which one of the following statements will be true for this circuit? It gives :

- a) correct reading for potential difference V but incorrect reading for current I.
- b) correct reading for current I but incorrect reading for potential difference V.
- c) correct readings for both I and V
- d) incorrect reading for current I as well as potential difference V.

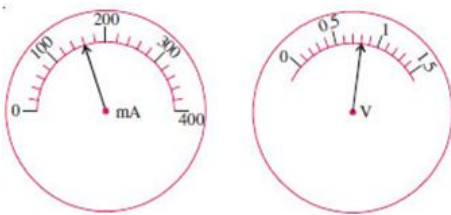
21. When performing the experiment on Ohm's law noted the milliammeter reading and voltmeter reading. From the obtained readings, the value of resistance calculated by him will be [1]



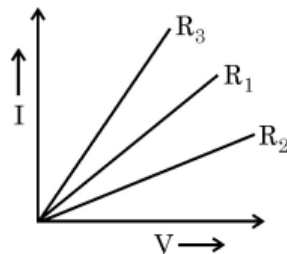- a) 5Ω
 - b) 0.005Ω
 - c) 0.5Ω
 - d) 0.05Ω
22. A student plots V-I graphs for three samples of nichrome wire with resistances R_1 , R_2 and R_3 . Choose from the following statement that holds true for this graph. [1]



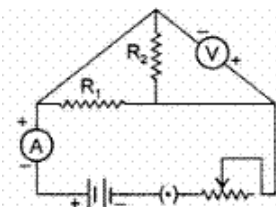- a) $R_2 > R_1 > R_3$
 - b) $R_1 > R_2 > R_3$
 - c) $R_1 = R_2 = R_3$
 - d) $R_3 > R_2 > R_1$
23. The only correct statement for the following electric is : [1]




- a) The Resistors R_1 and R_2 have been correctly connected in series.
 - b) The Resistors R_1 and R_2 have been correctly connected in parallel.
 - c) The Ammeter has been correctly connected in the circuit.
 - d) The Voltmeter has been correctly connected in the circuit.
24. Three resistors are shown in the figure. The resistance of the combination is: [1]



- [1]**




- [1]

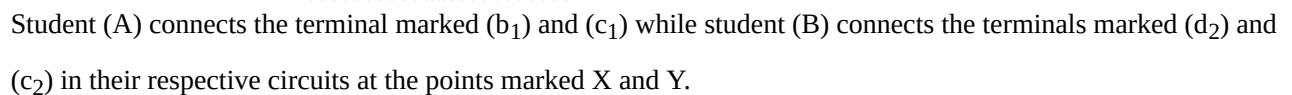


- Student (A) will determine the equivalent resistance of the series combination while student (B) will determine the equivalent resistance of the parallel combination of the two resistors.
- Both the students will determine the equivalent resistance of the parallel combination of the two resistors.
- Both the students will determine the equivalent resistance of the series combination of the two resistors.
- Student (A) will determine the equivalent resistance of the parallel combination while student (B) will determine the equivalent resistance of the series combination of the two resistors.

- [1]

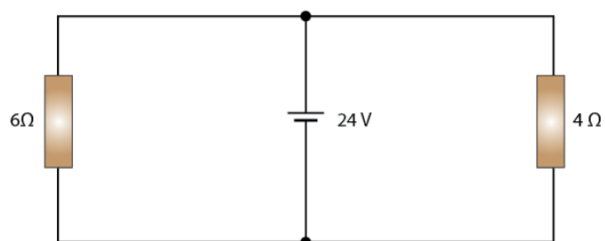


- a) 6 amp
b) 1 amp
c) 5 amp
d) None of these

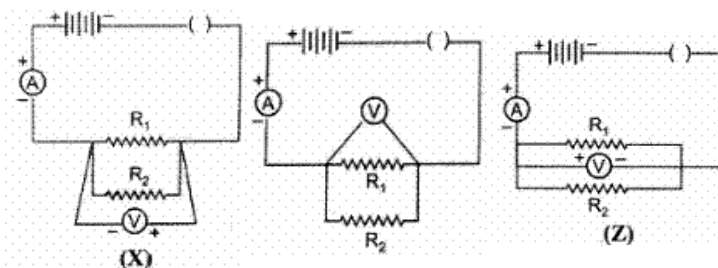28. In their experiment, on finding the equivalent resistance, of two resistors, connected in parallel, three students connected the voltmeter in their circuits, in the three ways X, Y, Z shown here. [1]




The voltmeter has been incorrectly connected in

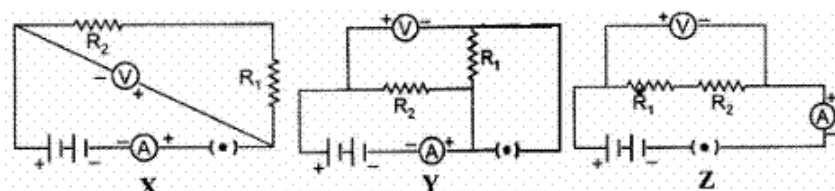- a) All the three cases
b) case X only
c) case Z only
d) case Y only
29. For determining the equivalent resistance of two resistors R_1 and R_2 connected in series, three student X, Y and Z set up their circuits as shown below. [1]




The correct set-up is that of

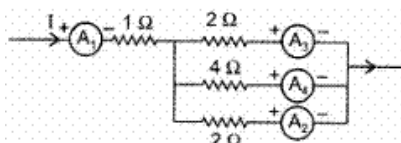- a) Student X only
b) Student Y only
c) Student X and Z
d) Student Z only
30. The ammeter showing the maximum current is : [1]



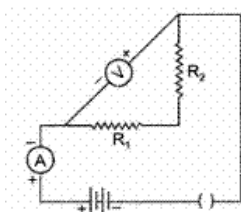
- a) A_1
b) A_4
c) A_3
d) A_2
31. For carrying out the experiment, on finding the equivalent resistance of two resistors, connected in parallel, a student sets up his circuit as shown. The teacher checks it and tells him that his circuit has one or more of the following 'faults'. [1]



- A. The resistors R_1 and R_2 have not been correctly connected in parallel.
 B. The voltmeter has not been correctly connected in the circuit.
 C. The ammeter and the key have not been correctly connected in the circuit.
 Out of these three, the actual fault in his circuit is/are


- a) Only A
 b) Only B
 c) Both B and C
 d) Both A and B

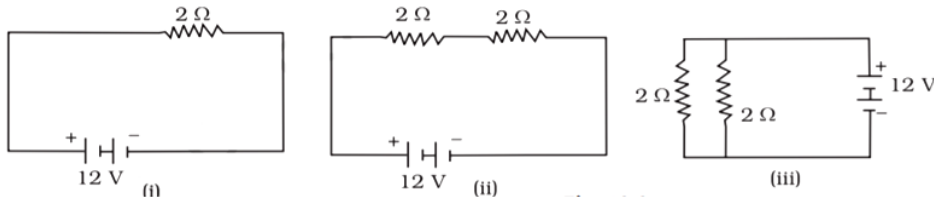32. In the following circuits (Figure), heat produced in the resistor or combination of resistors connected to a 12 V battery will be [1]



- a) Minimum in case (i)
 b) Same in all the cases
 c) Maximum in case (iii)
 d) Maximum in case (ii)

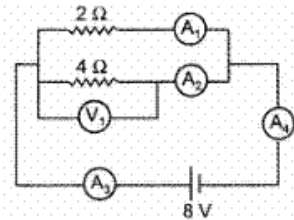
33. Using the given circuit with ammeter and voltmeter answer the question. [1]



The current indicated by A_3 is :

- a) 6A
 b) 2A
 c) 1A
 d) 4A

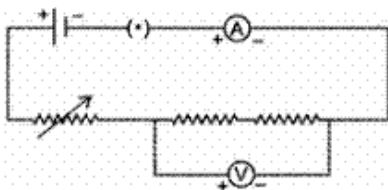
34. To determine the equivalent resistance of two resistors when connected in series, a student arranged the circuit components as shown in the diagram. But he did not succeed to achieve the objective. [1]



Which of the following mistakes has been committed by him in setting up the circuit ?

- a) Terminals of ammeter are wrongly connected.
 b) Terminals of voltmeter are wrongly connected.
 c) Position of voltmeter is incorrect
 d) Position of ammeter is incorrect

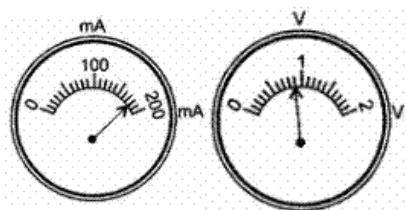35. The current flowing through a resistor and the potential difference developed across its ends are shown in the given diagrams : [1]




The value of resistance of the resistor is

- a) 500 ohm
- b) 0.5 ohm
- c) 50 ohm
- d) 5.0 ohm

36. The diagram below shows part of a circuit:

[1]

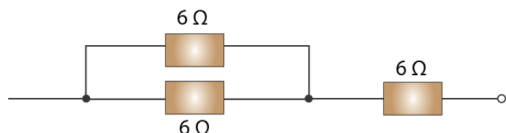


If this arrangement of three resistors was to be replaced by a single resistor, its resistance should be:

- a) 9 Ω
- b) 18 Ω
- c) 4 Ω
- d) 6 Ω

37. A student who wants to verify the equivalent resistance of two resistors R_1 and R_2 in series, attaches the end 1 and 2 of the voltmeter to three different pins of points in the given circuit. They are


[1]

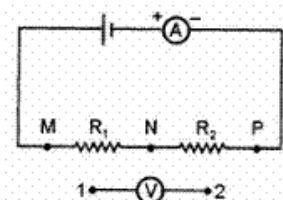

- a) [(1, M), (2, N)], [(1, N), (2, P)] and [(1, M), (2, P)]
- b) [(1, M), (2, N)], [(1, N), (2, P)] and [(1, N), (2, M)]
- c) [(1, M), (2, N)], [(1, P), (2, N)] and [(1, N), (2, M)]
- d) [(1, N), (2, P)], [(1, P), (2, N)] and [(1, N), (2, M)]

38. Out of the four given circuits for studying the dependence of the current on the potential difference across a resistor, the circuit that has been correctly drawn, is circuit


[1]

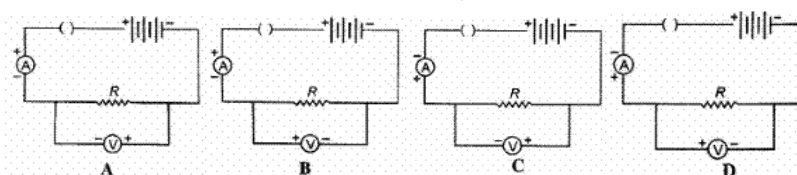

- a) A
- b) C
- c) D
- d) B


39. A student found that when a resistance of $3\ \Omega$ was joined with 3 V battery as per figure shown below, the current flowing through it was 1 A. He then joined another resistance of $6\ \Omega$ in parallel with $3\ \Omega$ resistance. The reading in the ammeter will now be:

[1]

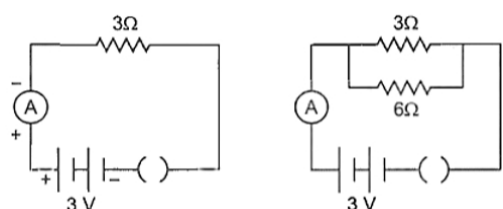


- a) 9 A
b) 1 A
c) 6 A
d) 1.5 A

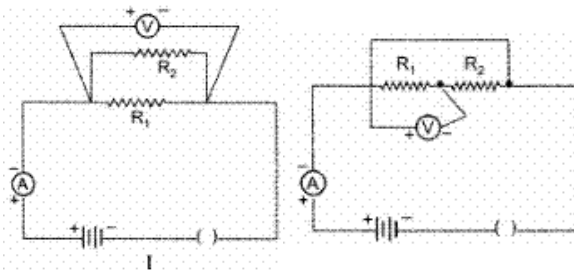40. Two students set up their circuits for finding the equivalent resistance of two resistors connected in parallel in two different ways as shown. [1]




The circuits likely to be labelled as correct :

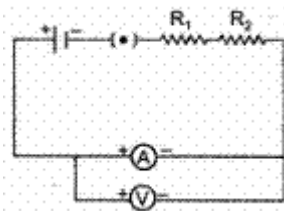
- a) are neither of the two circuits
b) are both the circuits
c) is only circuit I
d) is only circuit II
41. To determine the equivalent resistance of a series combination of two resistors R_1 and R_2 , a student arranges the following set-up :which one of the following statements will be true for this circuit ? [1]



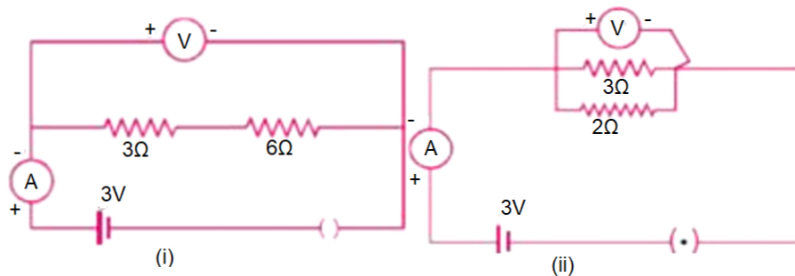- a) Incorrect reading for current I as well as potential difference V.
b) Correct reading for potential difference V but incorrect reading for current I
c) Correct reading for current I but incorrect reading for potential difference V.
d) Correct reading for both current I and potential difference V.
42. For the two circuits (i) and (ii) shown below the voltmeter reading would be [1]



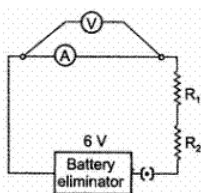- a) 0 V in case (i) and 2 V in case (ii)
b) 3 V in both the circuits
c) 3 V in case (i) and 0 V in case (ii)
d) 0 V in case (i) and 3 V in case (ii)
43. In an experiment, to find the equivalent resistance of a series combination of two resistors R_1 and R_2 a student used the circuit shown here. [1]



The circuit will give

- a) correct reading for current I, but incorrect
b) incorrect readings for both current I and

reading for voltage V


voltage V

c) correct reading for voltage V, but incorrect reading for current I

d) correct reading for both current I and voltage V

44. In the circuit shown below:

[1]

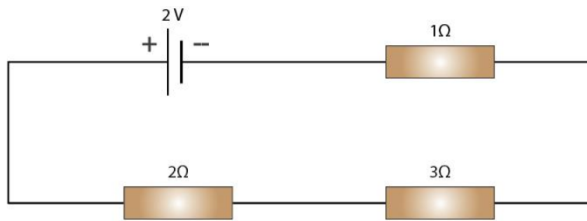

The potential difference across the 3Ω resistors is:

a) 2 V


b) $\frac{1}{9}$ V

c) $\frac{1}{2}$ V

d) 1 V

45. The proper representation of the series combination of cells (Figure) obtaining maximum potential is

[1]

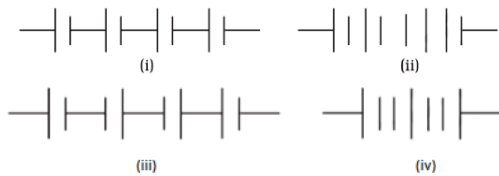

a) (i)


b) (iv)

c) (ii)

d) (iii)

46. Four different measuring instruments are shown below. Out of these, the instrument that can be used for measuring current is/are the instruments labelled as

[1]

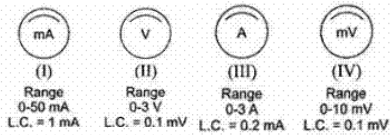

a) II and IV with IV more reliable of the two


b) II and III with II more reliable of the two

c) I and III with III more reliable of the two

d) I and IV with IV more reliable of the two

47. A student set up an electric circuit shown here for finding the equivalent resistance of two resistors in series. In this circuit, the

[1]

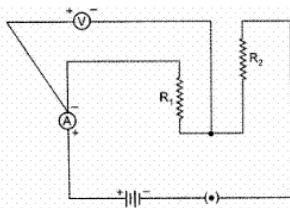

a) resistors, as well as the voltmeter, have been wrongly connected

b) resistors have been connected correctly but the voltmeter has been wrongly connected


c) resistors, as well as the ammeter, have been wrongly connected

d) resistors have been connected correctly but the ammeter has been wrongly connected

48. In the experiment on finding the equivalent resistance of two resistors, connected in parallel, two students connected the ammeter in two different ways as shown in given circuits I and II. The ammeter has been correctly

[1]

connected in

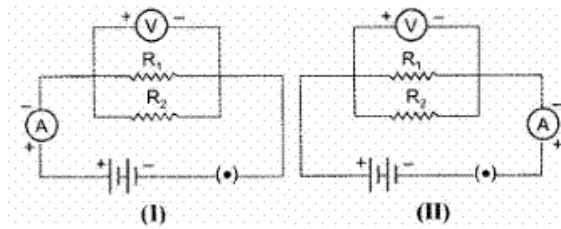


a) both the circuits (I) and (II)

b) circuit (II) only

c) circuit (I) only

d) neither of the two circuits.

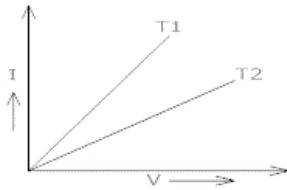49. $V - I$ graph for a metallic wire at two different temperatures T_1 and T_2 are shown in the following figure. Which of the two temperatures is higher? [1]




a) Temperature T_1

b) None of these

c) Temperature T_2

d) Temperature $T_1 = \text{Temperature } T_2$

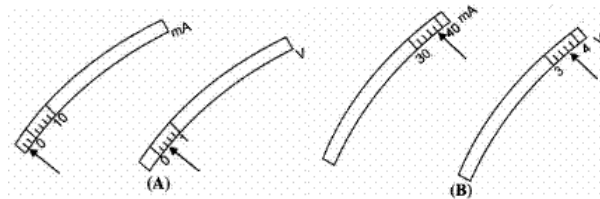50. The rest positions of the needles in a millimeter and voltmeter not in use are as shown in Fig a. when a student used these in his experiment, the readings of the needle are in the positions shown in Fig. B. The corrected values of current and voltage in the experiment are [1]




a) 34 mA and 4.0 V

b) 42 mA and 4.0 V

c) 34 mA and 3.2 V

d) 42 mA and 3.2 V

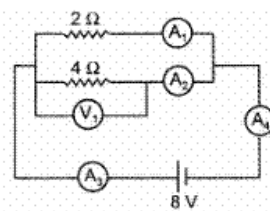51. Using the given circuit with ammeter and voltmeter answer the question. [1]



The ammeters showing same reading are :


a) A_3, A_4

b) A_1, A_2


c) A_1, A_3

d) A_2, A_4

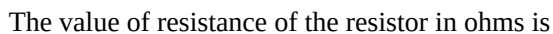52. The current flowing through a resistor connected in an electrical circuit and the potential difference developed across its ends are shown in the given diagrams : [1]



53. For three circuits, shown here

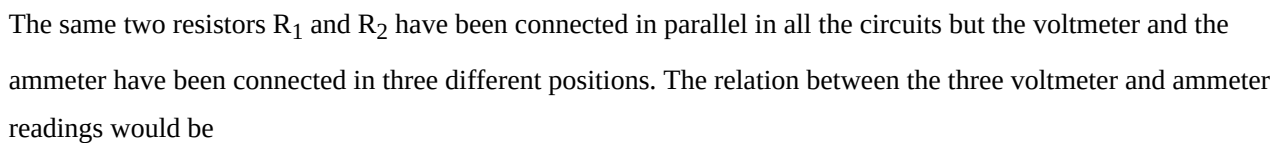


54. A cell, a resistor, a key, and an ammeter are arranged as shown in the circuit diagrams of the figure. The current recorded in the ammeter will be **[1]**



55. A student, using the same two resistors, battery, ammeter and voltmeter, sets up two circuits, connecting the two resistors, first in series and then in parallel. If the ammeter and voltmeter readings, in the two cases, are (I_1, I_2) and (V_1, V_2) respectively, he is likely to observe that



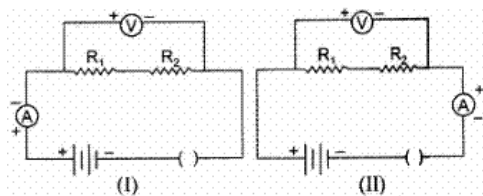
56. In the experiment on finding the equivalent resistance of two resistors, connected in series, the ammeter is correctly connected in: **[1]**



- a) neither of the two circuits. b) circuit (II) only
c) circuit (I) only d) both circuits (I) and (II)

57. The given diagram shows the milliammeter reading connected in a circuit :

[1]

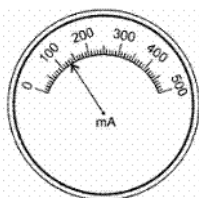


The value of current flowing in the circuit is

- a) 103 mA b) 160 mA
c) 100.3 mA d) 130 mA

58. A student sets up the circuit shown here for finding the equivalent resistance of two resistors, connected in series.


[1]

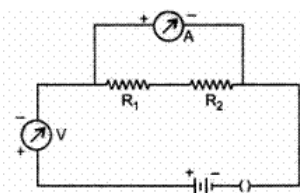

- a) the two resistors, the voltmeter and the ammeter have all been connected correctly b) the two resistors have been connected correctly but both the voltmeter and the ammeter have not been connected correctly.
c) the two resistors and the ammeter have been connected correctly, but the voltmeter has not been connected correctly. d) the two resistors and the voltmeter have been connected correctly but the ammeter has not been connected correctly.

59. Three batteries shown in the circuit has the emf of 2 V, 3 V, and 5 V correspondingly with an internal resistance of 1Ω . The external resistance of the circuit is 2Ω . Determine the value of the current I.

[1]

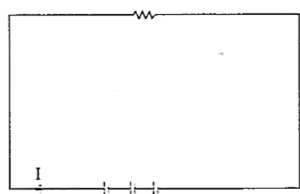

- a) 1.5 A b) 2.0 A
c) 2.5 A d) 3.1 A

60. From the shown figure, XY has a resistance of 35Ω , the potential difference across XY will be equal to _____.

[1]



-
- The figure shows four circuit diagrams, labeled 1, 2, 3, and 4, each containing a battery, a switch, and two resistors R_1 and R_2 connected in series.
- Circuit 1:** The voltmeter (V) is connected in parallel across the series combination of R_1 and R_2 . The ammeter (A) is connected in series with the resistors.
 - Circuit 2:** The voltmeter (V) is connected in parallel across the series combination of R_1 and R_2 . The ammeter (A) is connected in series with the resistors.
 - Circuit 3:** The voltmeter (V) is connected in parallel across the series combination of R_1 and R_2 . The ammeter (A) is connected in series with the resistors.
 - Circuit 4:** The voltmeter (V) is connected in parallel across the series combination of R_1 and R_2 . The ammeter (A) is connected in series with the resistors.


62. A student performs an experiment on studying the dependence of the current (I) flowing through a conductor on the potential difference (V) applied across it by setting up his circuit as shown. He records four values of ' T ' by keeping the sliding contact J , in the positions K , L , M and N , one by one. The corresponding points on his V - I graph are labelled as P_1 , P_2 , P_3 and P_4 . The point P_3 , would corresponding to the case when the sliding contact, J , is in the position




-
- The figure shows four circuit diagrams, labeled K, L, M, and N, each containing a battery, two resistors (R_1 and R_2), a voltmeter (V), and an ammeter (A).
- Diagram K:** The voltmeter (V) is connected in parallel across the battery. The ammeter (A) is connected in parallel across the series combination of R_1 and R_2 .
 - Diagram L:** The voltmeter (V) is connected in parallel across the series combination of R_1 and R_2 . The ammeter (A) is connected in series with the battery.
 - Diagram M:** The voltmeter (V) is connected in parallel across the battery. The ammeter (A) is connected in series with the series combination of R_1 and R_2 .
 - Diagram N:** The voltmeter (V) is connected in parallel across the series combination of R_1 and R_2 . The ammeter (A) is connected in parallel across the battery.

- a) L
b) N
c) K
d) M

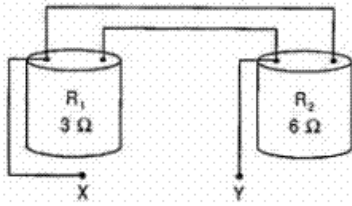64. The value of resistance marked on the two coils R_1 and R_2 are found to be correct. A student connects the given resistors in the following manner : [1]




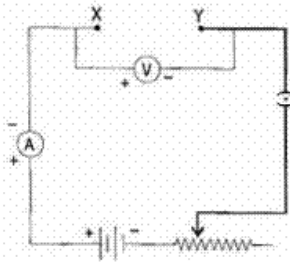He then connects the terminals marked X and Y above to the terminals marked X and Y in the circuit given below :




The average value of the ratio $\frac{V}{I}$ in the observations recorded in the above circuit would be :

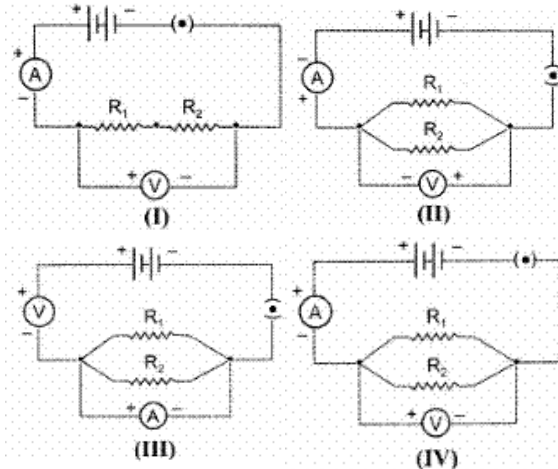- a) less than 3Ω
b) more than 6Ω
c) equal to 9Ω
d) between 3Ω and 6Ω
65. Following circuits were drawn by four students, to determine the equivalent resistance of two resistors when connected in parallel. The correct circuit is drawn by the student. [1]



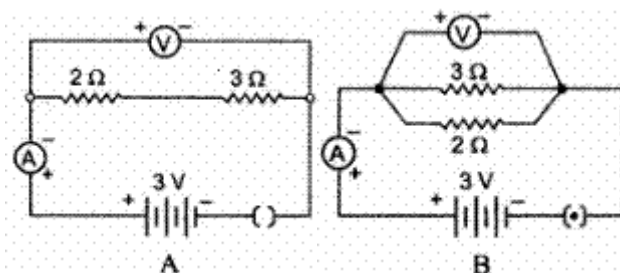- a) III
b) II
c) I
d) IV
66. For the circuits A and B shown below, find the voltmeter readings would be [1]




- a) 5 V in both circuits
b) 0 V in both circuits

c) 0 V in circuit A and 3 V in circuit B


d) 0.6 V in circuit A and 2.5 V in circuit B

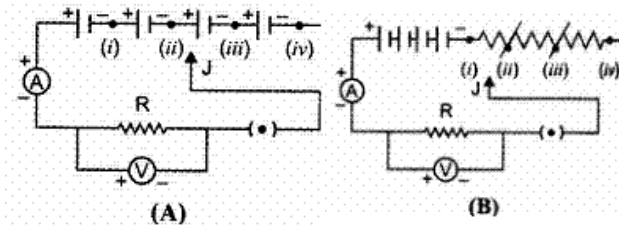67. To study the dependence of current (I) on the potential difference (V) across a resistor R, two students used the two set ups shown in Figure A and B respectively. They kept the contact point J in four different positions, marked (i), (ii), (iii) and (iv) in the two figures. [1]




For the two students, the ammeter and voltmeters readings will be maximum when the contact J is in the position

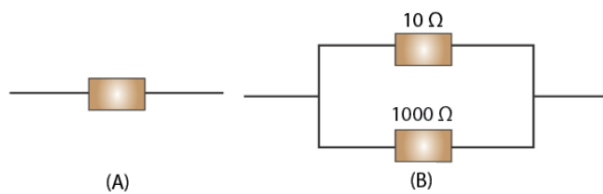
- a) (iv) in set up A and (i) in set up B
b) (i) in both the set ups
c) (iv) in both the set ups
d) (i) in set up A and (iv) in set up B
68. Which of the following resistor arrangement, A or B, has the lower combined resistance? [1]



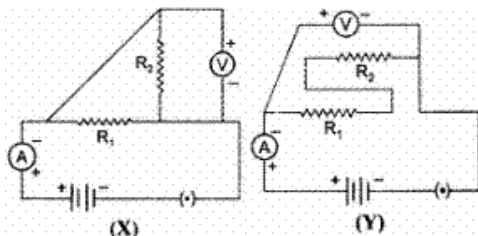- a) 9.9
b) None of these
c) 9.0
d) 9.5
69. The only correct statement for the two circuits (X) and (Y) shown below is : [1]



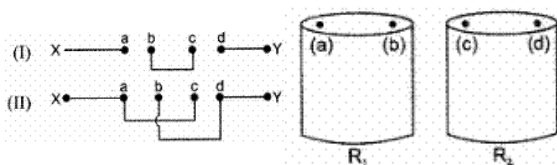- a) The resistors R_1 and R_2 have been connected in parallel in both the circuits.
b) The resistors R_1 and R_2 have been connected in series in both the circuits.
c) In the circuit (X) the resistors have been connected in parallel whereas these are connected in series in circuit (Y)
d) In the circuit (X) the resistors R_1 and R_2 are connected in series while these are connected in parallel in circuit (Y).
70. Two resistors R_1 and R_2 have their terminals marked as (a), (b), (c) and (d) as shown. A student connects these terminals to one another in two different ways shown below : [1]



The equivalent resistance between the points X and Y in the two cases, are measured to be R' and R'' respectively. We can then say that

- a) Both R' and R'' are equivalent to the parallel
b) R' is equivalent to the parallel combination

combination of R_1 and R_2


of R_1 and R_2 and R'' is equivalent to the series combination of R_1 and R_2

c) R' is equivalent to the series combination of R_1 and R_2 , R'' is equivalent to the parallel combination of R_1 and R_2

d) Both R' and R'' are equivalent to the series combination of R_1 and R_2

71. While doing their experiment, on finding the equivalent resistance, of two resistor connected in series, three students A, B, C set up their circuits as shown below :

[1]

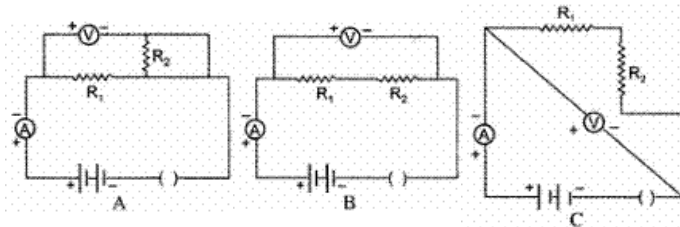


The correct set up is that of

- a) Student B and C
b) Student A and B
c) Student B, C and A
d) Student C and A

72. For the circuit arrangement, show below, the student would observe


[1]

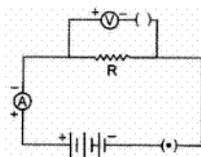

- a) some reading in the voltmeter but no reading in the ammeter
b) no reading in either the ammeter or the voltmeter
c) some reading in the ammeter but no reading in the voltmeter
d) some reading in both the ammeter and the voltmeter

73. In the experiments on finding the equivalent resistance of two resistors, connected in parallel, three students connected the voltmeter in their circuits, in the three ways, X, Y and Z shown here.

[1]

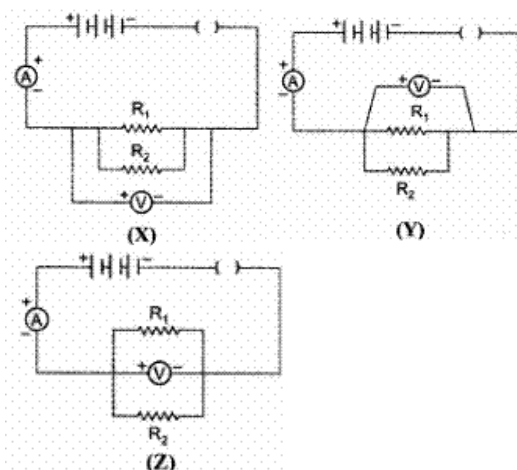


The voltmeter has been correctly connected in

- a) cases Z and X only
b) cases X and Y only
c) cases Y and Z only
d) all X, Y and Z cases


74. The values of resistance marked on the coils R_1 and R_2 are found to be correct. A student connects the given

[1]

resistors in the following manner.

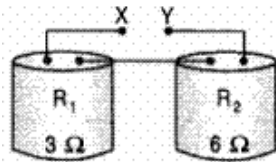

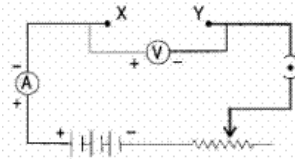He then connects the terminals marked X and Y above to the terminals marked X and Y in the circuit.




The average value of the ratio $\frac{V}{I}$ in the observations recorded in the circuit would be :

- a) 2Ω
- b) 6Ω
- c) 9Ω
- d) 3Ω

75. Which of the circuit components in the following circuit diagram are connected in parallel ?

[1]

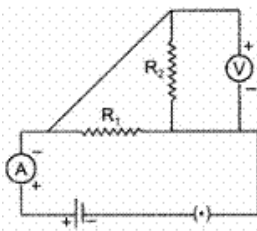

- a) R_1 and V only
- b) R_1 and R_2 only
- c) R_1 , R_2 and V
- d) R_2 and V only