



ELECTRICITY -11

Class 10 - Science

Section A

1. **State True or False:** [19]
- (a) A conductor having some appreciable resistance is called a resistor. [1]
 - (b) A continuous and closed path of an electric current is called an electric circuit. [1]
 - (c) In circuits using metallic wires, electrons constitute the flow of charges. [1]
 - (d) One ampere is constituted by the flow of one coulomb of charge per second. [1]
 - (e) Tungsten is used almost exclusively for filaments of electric bulbs. [1]
 - (f) When current is passed through a high resistance wire, the wire becomes very hot and produces heat, this effect is known as the heating effect of current. [1]
 - (g) A switch makes a conducting link between the cell and the bulb. [1]
 - (h) The electric potential difference between two points in an electric circuit, carrying some current, is the amount of work done to move a unit charge from one point to another. [1]
 - (i) In an electric circuit, a device called rheostat is often used to change the resistance in the circuit. [1]
 - (j) Copper and aluminium are generally used for electrical transmission lines. [1]
 - (k) Voltmeter is a device used for the measurement of current. [1]
 - (l) The potential difference is measured by means of an instrument called the galvanometer. [1]
 - (m) A drawing showing the way various electric devices are connected in a circuit is called a circuit diagram. [1]
 - (n) The ammeter is always connected in parallel across the points between which the potential difference is to be measured. [1]
 - (o) The motion of electrons in an electric circuit constitutes an electric current. [1]
 - (p) The property of the conduct due to which it opposes the flow of current through it is called resistance of the conductor. [1]
 - (q) When an electrical appliance consumes electrical energy at the rate of 1 joule per second, its power is said to be 1 watt. [1]
 - (r) A series circuit divides the current through the electrical gadgets. [1]
 - (s) A component used to regulate current without changing the voltage source is called variable resistance. [1]

Section B

2. **Fill in the blanks:** [20]
- (a) When current is passed through a high resistance wire, the wire becomes very hot and produces heat, this effect is known as _____ of current. [1]
 - (b) The conventional direction of electric current is the one in which _____ charges move orderly. [1]

- (c) The commercial unit of electric energy is _____. [1]
- (d) A continuous and closed path of an electric current is called an _____. [1]
- (e) When an electrical appliance consumes electrical energy at the rate of 1 joule per second, its power is said to be _____. [1]
- (f) _____ is used almost exclusively for filaments of electric bulbs. [1]
- (g) The S.I. unit of _____ is ohm metre. [1]
- (h) In an electric circuit, a device called _____ is often used to change the resistance in the circuit. [1]
- (i) A _____ showing the way various electric devices are connected in a circuit is called a circuit diagram. [1]
- (j) _____ is the rate at which electrical energy is produced or consumed in an electric circuit. [1]
- (k) Those substances through which electricity cannot flow are known as _____. [1]
- (l) The potential difference is measured by means of an instrument called the _____. [1]
- (m) A component used to regulate the current without changing the voltage source is called _____. [1]
- (n) A _____ circuit divides the current through the electrical gadgets. [1]
- (o) A conductor having some appreciable resistance is called a _____. [1]
- (p) _____ is a device used for the measurement of current. [1]
- (q) A component of identical size that offers a _____ resistance is a poor conductor. [1]
- (r) _____ states that at a constant temperature, the current flowing through a conductor is directly proportional to the potential difference across its ends. [1]
- (s) The _____ at a point in a field is defined as the work done in moving a unit charge from infinity to that point. [1]
- (t) One _____ is constituted by the flow of one coulomb of charge per second. [1]

Section C

3. Which of the given statement is true or false: [1]
Statement A: Resistivity increases with a decrease in temperature in insulators.
Statement B: Resistivity of a conductor increases with increasing temperature.
- a) Statement A is true, Statement B is false. b) Neither statement A nor statement B is true.
 c) Statement A is false, Statement B is true. d) Both the statements A and B are true.
4. Which of the given statement is true or false: [1]
Statement A: Light from a bathroom bulb gets dimmer for a moment when the geyser is switched on.
Statement B: Insulators conduct charges, they can be charged easily by friction.
- a) Both the statements A and B are true. b) Neither statement A nor statement B is true.
 c) Statement A is true; Statement B is false. d) Statement B is true; Statement A is false.
5. A student performing an experiment with a series combination of two resistors infers that [1]
A: Potential difference across the combination is the sum of the potential difference across each of them.
B: The current passing through them is the same.
 Which of the following statement is/are true?
- a) Both A and B are false b) B is true and A is false
 c) A is true and B is false d) Both A and B are true
6. When two objects are rubbed together, one object loses some of its free electrons while the other gains the same [1]

A. The object losing electrons.
B. The object gaining electrons.

Section D

c) A and C

d) A and D

12. Which statement/statements is/are correct?

[1]

a) A voltage has a low resistance

b) An ammeter is connected in series in a circuit and a voltmeter is connected in parallel

c) An ammeter has a high resistance

d) None of these

Section E

13. A student uses a battery of adjustable voltage 0-6 V. she has to perform an experiment to determine the equivalent resistance of two resistors when connected in parallel using two resistors of value 3 ohm and 6 ohm. The best choice of combination of voltmeter and ammeter to be used in the experiment is

[1]

a) Ammeter of range 0-5 A and voltmeter of range 0-2 V.

b) Ammeter of range 0-2 A and voltmeter of range 0-10 V.

c) Ammeter of range 0-5 A and voltmeter of range 0-5 V.

d) Ammeter of range 0-5 A and voltmeter of range 0-10 V

14. The following apparatus is available in the laboratory

[1]

Battery: adjustable from 0 to 6 V

Resistors: 4Ω and 12Ω

Ammeters: A_1 and Range 0 to 5 A; Least Count 0.25 A; A_2 and Range 0 to 3 A; Least Count 0.1 A

Voltmeters: V_1 of Range 0 to 10 V; Least Count 0.5 V; V_2 of Range 0 to 5 V; Least Count 0.1 V

For the experiments to find the equivalent resistance of the parallel combination of the two given resistors, the best choice would be:

a) ammeter A_2 and voltmeter V_1

b) ammeter A_2 and voltmeter V_2

c) ammeter A_1 and voltmeter V_2

d) ammeter A_1 and voltmeter V_1

15. In an experiment on finding the equivalent resistance of two resistors, connected in series, a student connects the terminals of the voltmeter, to

[1]

a) both the terminals of each of the two resistors.

b) both the terminals of one resistor and one terminal of the other resistor.

c) one terminal of each of the two resistors and these terminals are also interconnected.

d) one terminal of each of the two resistors and these terminals are not interconnected.

16. The following precautions were listed by a student in the experiment on study of Dependence of current on potential difference.

[1]

A. Use copper wires as thin as possible for making connections.

B. All the connections should be kept tight.

C. The positive and negative terminals of the voltmeter and the ammeter should be correctly connected.

D. The zero error in the ammeter and the voltmeter and the voltmeter should be noted and taken into consideration while recording the measurements.

E. The key in the circuit, once plugged in, should not be taken out till all the observations have been completed.

The precautions that need to be corrected and revised are:

- a) B and E
b) A, C and E
c) A and E
d) C and E

17. A student did the experiment to find the equivalent resistance, of two given resistors, R_1 and R_2 , first when they are connected in series and next when they are connected in parallel. The two values of the equivalent resistance obtained by him were R_S and R_P respectively. He would find that [1]

a) $R_S > R_P$
b) $R_P > R_S$
c) $R_S = R_P$ but not equal to $\frac{R_1 + R_2}{2}$
d) $R_S = R_P = \frac{R_1 + R_2}{2}$

18. The following apparatus is available in a laboratory. [1]
Cell: Adjustable from 0 to 1.5 volt
Resistor: 4Ω and 12Ω
Ammeters: A_1 of Range 0 to 3 A; Least Count 0.01 A : A_2 of Range 0 to 1 A; Least Count 0.05 A
Voltmeters: V_1 of Range 0 to 10 V; Least Count 0.5 V: V_2 of Range 0 to 5 V; Least Count 0.1 V
The best combination of voltmeter and ammeter for finding the equivalent resistance of the resistors in parallel would be

a) ammeter A_1 and voltmeter V_1
b) ammeter A_2 and voltmeter V_2
c) ammeter A_2 and voltmeter V_1
d) ammeter A_1 and voltmeter V_2

19. Three students X, Y and Z, while performing the experiment to study the dependence of current on the potential difference across a resistor, connect the ammeter (A), the battery (B), the key (K) and the resistor (R), in series, in the following three different orders. [1]
 $X \longrightarrow B, K, R, A, B$
 $Y \longrightarrow B, A, K, R, B$
 $Z \longrightarrow B, R, K, A, B$
Who has connected them in the correct order?

a) Z
b) X
c) X, Y and Z
d) Y

20. The following instruments are available in a laboratory :Milliammeter A_1 of range 0-300 mA and least count 10 mA
Milliammeter A_2 of range 0-200 mA and least count 20 mA
Voltmeter V_1 of range 0-5 V and least count 0.2 V
Voltmeter V_2 of range 0-3 V and least count 0.3 V. [1]
Out of the following pairs of instruments, which pair would be the best choice for carrying out the experiment to determine the equivalent resistance of two resistors connected in series ?

a) Milliammeter A_2 and voltmeter V_2
b) Milliammeter A_1 and voltmeter V_1
c) Milliammeter A_2 and voltmeter V_1
d) Milliammeter A_1 and voltmeter V_2

A student did the experiment to find the equivalent resistance, of two given resistors, R_1 and R_2 , first when they are connected in series and next when they are connected in parallel. The two values of the equivalent resistance obtained by him were R_S and R_P respectively. He would find that

- a) $R_S > R_P$
- b) $R_P > R_S$
- c) $R_S = R_P$ but not equal to $\frac{R_1 + R_2}{2}$
- d) $R_S = R_P = \frac{R_1 + R_2}{2}$

18. The following apparatus is available in a laboratory. [1]

Cell: Adjustable from 0 to 1.5 volt

Resistor: 4Ω and 12Ω

Ammeters: A_1 of Range 0 to 3 A; Least Count 0.01 A : A_2 of Range 0 to 1 A; Least Count 0.05 A

Voltmeters: V_1 of Range 0 to 10 V; Least Count 0.5 V; V_2 of Range 0 to 5 V; Least Count 0.1 V

The best combination of voltmeter and ammeter for finding the equivalent resistance of the resistors in parallel would be

- a) ammeter A_1 and voltmeter V_1 b) ammeter A_2 and voltmeter V_2
c) ammeter A_2 and voltmeter V_1 d) ammeter A_1 and voltmeter V_2

19. Three students X, Y and Z, while performing the experiment to study the dependence of current on the potential difference across a resistor, connect the ammeter (A), the battery (B), the key (K) and the resistor (R), in series, in the following three different orders. **[1]**

$$X \longrightarrow B, K, R, A, B$$
$$Y \longrightarrow B, A, K, R, B$$
$$Z \longrightarrow B, R, K, A, B$$

Who has connected them in the correct order?

- a) Z b) X
c) X, Y and Z d) Y


20. The following instruments are available in a laboratory :Milliammeter A_1 of range 0-300 mA and least count 10 mA
Milliammeter A_2 of range 0-200 mA and least count 20 mA
Voltmeter V_1 of range 0-5 V and least count 0.2 V
Voltmeter V_2 of range 0-3 V and least count 0.3 V.

Out of the following pairs of instruments, which pair would be the best choice for carrying out the experiment to determine the equivalent resistance of two resistors connected in series ?


- a) Milliammeter A_2 and voltmeter V_2
- b) Milliammeter A_1 and voltmeter V_1
- c) Milliammeter A_2 and voltmeter V_1
- d) Milliammeter A_1 and voltmeter V_2

21. a. What is the heating effect of electric current? [3]
b. Write an expression for the amount of heat produced in a resistor when an electric current is passed through it stating the meanings of the symbols used.
c. Name two appliances based on heating effect of electric current.

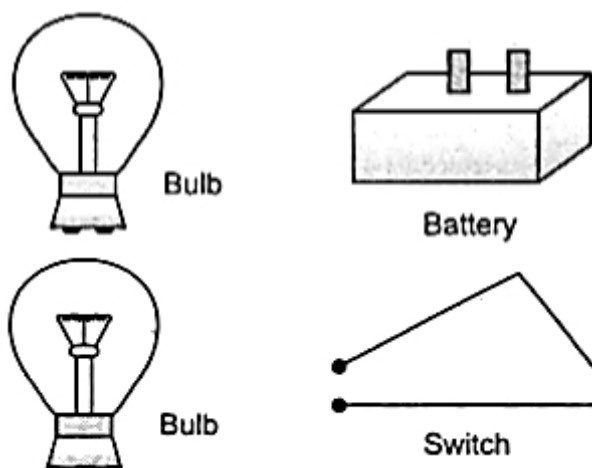
22. Judge the equivalent resistance when the following are connected in parallel (a) 1Ω and $10^6\Omega$ (b) 1Ω and $10^3\Omega$ and $10^6\Omega$ [3]
23. The given figure shows a battery, a switch and two bulbs. Complete the diagram to show the electric connections of the bulbs to the battery. How have you joined the bulbs? Give a reason. [3]



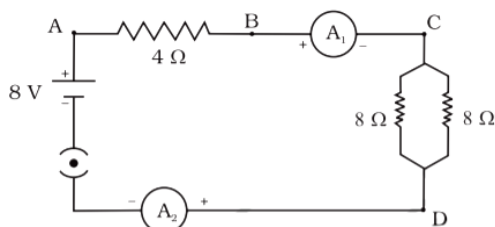
24. Find out the following in the electric circuit given in Figure [3]




- The potential difference across 4Ω resistance
 - The power dissipated in 4Ω resistor
25. A metallic wire of resistance R is cut into ten parts of equal length. Two pieces each are joined in series and then five such combinations are joined in parallel. What will be the effective resistance of the combination? [3]
26. Five resistors are connected in a circuit as shown in figure. Find the ammeter reading when the circuit is closed. [3]

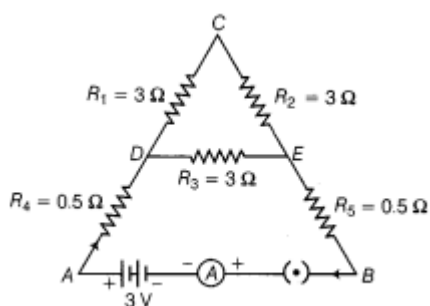

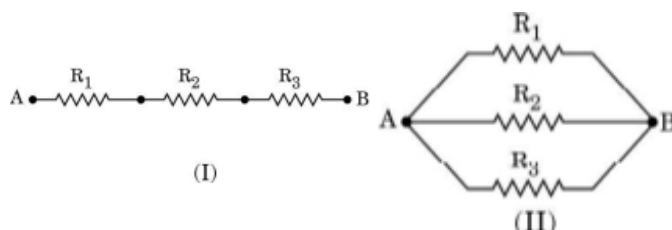27. i. Write the formula for determining the equivalent resistance between A and B of the two combinations (I) and (II) of three resistors R_1 , R_2 and R_3 arranged as follows: [3]



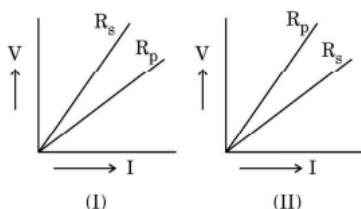- If the equivalent resistance of the arrangements (I) and (II) are R_s and R_p respectively, then which one of the following VI graphs is correctly labelled? Justify your answer.




28. Calculate the total cost of running the following electrical devices in the month of September, if the rate of 1 unit of electricity is Rs. 6.00. [3]


- Electric heater of 1000 W for 5 hours daily.
- Electric refrigerator of 400 W for 10 hours daily.

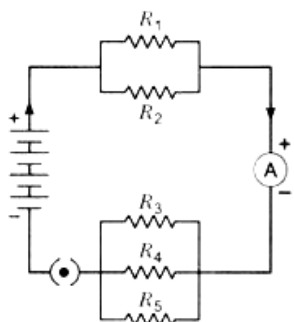29. If in the figure $R_1 = 10\Omega$, $R_2 = 40\Omega$, $R_3 = 30\Omega$, $R_4 = 20\Omega$, $R_5 = 60\Omega$, and a 12 V battery is connected to the arrangement. Calculate [3]


- the total resistance in the circuit, and
- the total current flowing in the circuit.



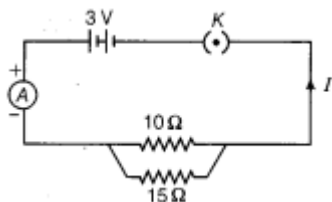30. Study the following circuit and answer the questions that follows: [3]



- How much current is flowing through
 - 10Ω and
 - 15Ω resistor?
 - What is the ammeter reading?
31. a. List the factors on which the resistance of a uniform cylindrical conductor of a given material depends. [3]
 b. The resistance of a wire of 0.01 cm radius is 10Ω . If the resistivity of the wire is $50 \times 10^{-8} \Omega\text{m}$, find the length of this wire.
32. Show how would you join three resistors, each of resistance 9Ω so that the equivalent resistance of the combination is [3]
 i. 13.5Ω
 ii. 6Ω ?
33. i. When a 12 V battery is connected across an unknown resistor, there is a current of 2.5 mA in the circuit. Find the value of the resistance of the resistor? [3]
 ii. 320J of heat is produced in 10 s in a 2Ω resistor. Find the amount of current flowing through the resistor.
34. In the diagram given below, Coil - 1 is connected in series with a battery and a plug key while Coil - 2 is connected with a galvanometer. [3]

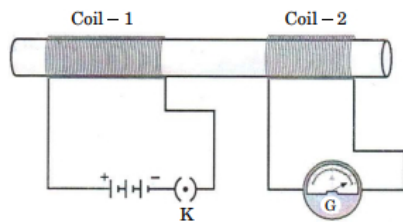

- Why does the galvanometer show deflection only when the key (K) is plugged in and not when a steady current starts flowing in the circuit?
- What is observed in the galvanometer, when the key is plugged out?
- State the conclusion based on the observation of this activity.

35. Three students X, Y and Z while performing the experiment to study the dependence of current on the potential difference across a resistor, connect the ammeter (A), the battery (B), the key (k) and the resistor (R) in series, in the following three different orders. [3]


- $X \rightarrow B, K, R, A, B$
- $Y \rightarrow B, A, K, R, B$
- $Z \rightarrow B, R, K, A, B$

Who has connected them in the correct order?

36. i. An electric iron consumes energy at a rate of 840 W when heating is at the maximum rate and 360 W when the heating is at the minimum rate. The applied voltage is 220 V. What is the value of current and the resistance in each case? [3]
- ii. Which uses more energy, a 250 W TV set for 1 hour or a 1,200 W toaster for 10 minutes?

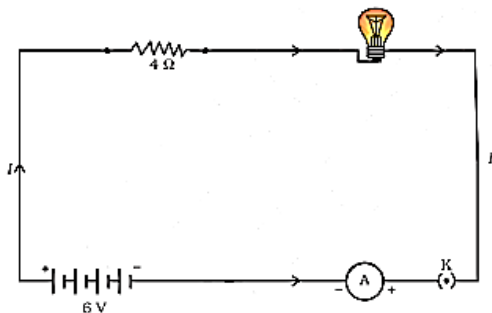37. An electric lamp, whose resistance is 20Ω , and a conductor of 4Ω resistance are connected to a 6 V battery in figure. [3]

Calculate (a) the total resistance of the circuit, (b) the current through the circuit, and (c) the potential difference across the electric lamp and conductor.



38. i. A hot plate of an electric oven connected to a 220 V line has two resistance coils A and B, each of 24Ω resistance, which may be used separately, in series, or in parallel. What are the currents in the three cases? [3]
- ii. Calculate the resistance of an electric bulb that allows a 10A current when connected to a 220V power source?